



Contents

1	Power Supply Systems	
1.1	Introduction - Electrical Safety	8-1-1
1.2	General	8-1-1
1.3	Definitions	8-1-3
1.4	Power Unit Requirements	8-1-3
1.5	Low Voltage Overload Protection	8-1-3
1.6	Supply Voltage	8-1-4
1.7	Single Controller Supply System	8-1-4
1.8	Multiple Controller Supply System	8-1-4
1.8.1	Individual mains fed controllers	8-1-4
1.8.2	Single power supply feeding all controllers	8-1-6
1.8.3	Split potential supply	8-1-6
1.9	Three Rail Systems	8-1-6
1.10	Selection of Controller and Power Supply Unit Capacity	8-1-8
1.11	Controller Output Cable Sizes	8-1-9
1.12	Controller Output Meters	8-1-10
1.13	Interpreting Meter Readings	8-1-13
Tables		
Table 1	Wire Resistance	8-1-10
Inserts		
	Rectification	8-1-2
	Transformer Regulation	8-1-8
Data Sheet		
D8.1.1	Electrical Symbols (<i>Ex E1 / 1</i>)	D8.1.1
2	Speed and Direction Control	
2.1	General	8-2-1
2.2	Speed Control	8-2-1
2.2.1	Rheostat control	8-2-1
2.2.2	Electronic control	8-2-3
2.3	Direction Control	8-2-4
2.3.1	DC Permanent magnet motors	8-2-5
2.3.2	Wound field motors	8-2-5
Insert		
	Rheostat Control	8-2-5
3	Turnout Wiring	
3.1	Two Rail Turnouts	8-3-1
3.2	Three Rail Turnouts	8-3-3
3.3	Self Isolating Turnouts	8-3-4
3.3.1	Multiple sidings	8-3-5
3.3.2	Loops	8-3-5
3.3.3	Safety dead sections	8-3-6
3.3.4	Heel fed points	8-3-7
3.3.5	Slips, diamonds, multiple crossings	8-3-8
4	Small Layout Wiring	
4.1	General	8-4-1
4.2	A Simple Loop Terminus	8-4-2
4.3	Goods Sidings	8-4-5
4.4	A Typical Branch Line Terminus	8-4-5
4.5	Two Trains at Once	8-4-7
4.6	Route Selection	8-4-8
4.7	Three Rail Wiring	8-4-10

5	Multiple Controls	
5.1	Introduction	8-5-1
5.2	Area Control and Control Linking	8-5-1
5.2.1	Point to point – single track main line	8-5-1
5.2.2	Link switching – single track main line	8-5-1
5.2.3	Simple indicating system	8-5-2
5.2.4	Intermediate station – single track main line	8-5-3
5.2.5	Point to point - double track main line	8-5-3
5.2.6	Intermediate area – double track main line	8-5-4
5.2.7	Linking three-rail areas	8-5-4
5.3	Cab control	8-5-5
5.3.1	Zone control	8-5-5
5.4	Loco Borne Control (<i>in preparation</i>)	
6	Return Track and Triangular Junction Wiring	
6.1	Introduction	8-6-1
6.2	Return Track Configuration	8-6-2
6.3	Point to Loop	8-6-2
6.3.1	Single track loop	8-6-2
6.3.2	Polarity indication	8-6-3
6.3.3	Single track loop with triangular junction	8-6-3
6.4	Double track loop	8-6-5
6.5	Loop to Loop or Dogbone	8-6-7
6.6	Double Track Loop with Y Junction	8-6-8
6.7	Double Track Loop with Triangular Junction	8-6-8
6.8	Oval Layout Return Track	8-6-11
6.9	Scissors Crossovers	8-6-12
6.9.1	Route setting via scissors crossovers	8-6-12
7	Tracing Electrical Faults	
7.1	General	8-7-1
7.1.1	Test equipment	8-7-1
7.2	Supply System fault Diagnosis	8-7-1
7.2.1	Power unit failure	8-7-1
7.2.2	Open circuit	8-7-2
7.2.3	Short circuit	8-7-2
7.2.4	Check for partial short circuit	8-7-3
7.2.5	High circuit resistance	8-7-3
7.2.6	Loss of control	8-7-4
7.3	Train Fault Diagnosis	8-7-4
7.3.1	Rolling stock	8-7-4
7.3.2	Locomotive	8-7-4
7.3.3	Motor defects	8-7-5
7.4	Some case histories	8-7-6
7.4.1	Faulty pick-up	8-7-6
7.4.2	Faulty micro-switch operation	8-7-6
7.4.3	Backstairs or ‘Sneak’ circuit	8-7-6
7.4.4	Flangeway problem	8-7-6
7.4.5	Feeder failure	8-7-6